



The Co-operative University of Kenya

END OF SEMESTER EXAMINATIONS DECEMBER-2019

EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN COMPUTER

SCIENCE

(YR IV SEM II)

UNIT CODE: BCSC 1138

UNIT TITLE: ELECTRONICS I

DATE: 9th DECEMBER 2019

TIME: 9:00 AM – 11:00 AM

INSTRUCTIONS:


Answer question **ONE** (**compulsory**) and any other **TWO** questions

QUESTION ONE

- (a) Giving examples differentiate between passive and active electronic circuit components (4 marks)
- (b) Explain the following electronic circuit elements (6 marks)
 - i. Capacitor
 - ii. Inductor
 - iii. Diode
- (c) Using a neat diagram explain the I-V characteristics of a PN Junction diode (8 marks)
- (d) Explain how the potential barrier is developed on PN junction (4 marks)
- (e) Using a neat diagram explain the **THREE** operation regions of a BJT. State the application of BJT in each region (7 marks)

QUESTION TWO

 
- (a) Explain how the depletion layer is formed on the PN junction (2 marks)
- (b) Differentiate between intrinsic and extrinsic semiconductors (4 marks)
- (c) Using Thevenin`s Theorem calculate the voltage drop across the 2Ω resistor in the circuit shown below (8 marks)



- (d) With the aid of diagrams, describe any two bipolar transistor biasing methods (6 marks)

QUESTION THREE

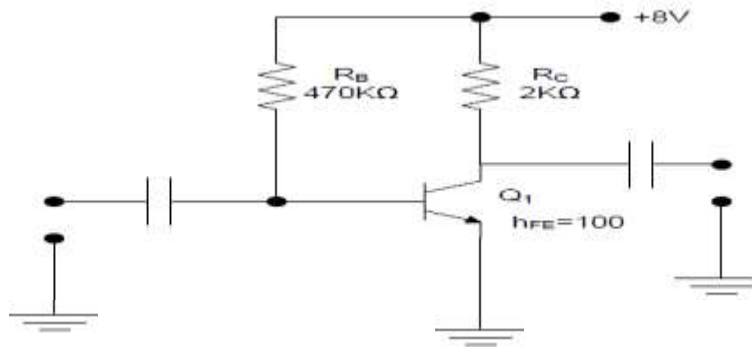- (a) State the structural and functional difference between NPN and PNP transistors (6 marks)
- (b) In an NPN transistor 10^8 holes/ μ s move from the base to the emitter region while 10^{10} electrons/ μ s move from the emitter to the base region. An ammeter reads the base current as $I_B = 16\mu$ A. Determine the Emitter Current I_E and the collector current I_C . (4 marks)
- (c) For the diagram of figure 3 below, determine:
- Configuration of the transistor amplifier (2 marks)
 - Q-point (Values of I_C and V_{CE}) (3 marks)
 - Draw the DC load line (Label the value of the quiescent base current curve, I_B , and mark the Q-point.) (3 marks)



- (d) Explain how the drain current is controlled in n-channel JFETs? (2 marks)

QUESTION FOUR

- (a) Using a well labeled diagram, describe the working of an N-channel JFET. (12 marks)
- (b) Using a neat diagram explain the voltage divider bias of a BJT. Show the expression for transistor collector voltage and collector emitter voltage (8marks)

QUESTION FIVE

- (a) Explain the source of charge carriers in intrinsic semiconductors (2 marks)
- (b) Explain the difference between JFET and MOSFET (4 marks)
- (c) Draw the symbols for N-channel MOSFET and P-Channel MOSFET (4 marks)
- (d) Explain three reasons why a JFET is preferred over a BJT (6 marks)
- (e) Describe the characteristics of the JFET when operated in the ohmic region. (4 marks)